

1. The signal  $x(t) = 5\sin(15t - 60^\circ) + 2\sin(7t)$  is periodic in

- A.  $\pi$
- B.  $15/7$
- C.  $15\pi$
- D.  $2\pi$

2. What is the function of the TTL gate shown below


A.  $(\bar{A} \cdot B) + (\bar{C} \cdot D)$

B.  $\overline{(\bar{A} \cdot B) + (\bar{C} \cdot D)}$

C.  $(A \cdot \bar{B}) + (C \cdot \bar{D})$

D.  $\overline{(A \cdot \bar{B}) + (C \cdot \bar{D})}$

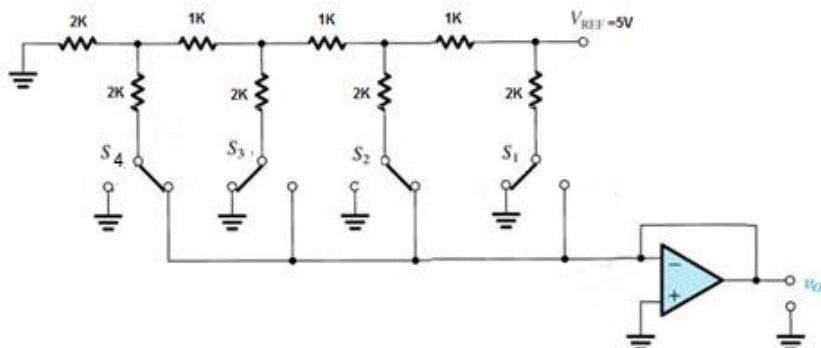3. For the R-2R ladder shown below. What is the output voltage ? (check the state of the switches)



- A.  $2.500V$
- B.  $0.3125V$
- C. **1.5625V**
- D.  $3.1250V$