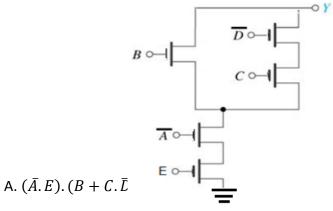
- 1. If more resistors are added in a series circuit resistance will be
  - A. increased
  - B. decreased
  - C. equal
  - D. constant
- 2. In the state space model of a dynamic system with matrices A, B, C and D, what is the matrix B also called?
  - A. Direct transmission matrix.
  - B. Input (or control) matrix.
  - C. State matrix.
  - D. Output matrix.
- 3. Which function corresponds to the following pull-down-network



- B.  $(\bar{A} + E) + (B.(C + \bar{D}))$
- C.  $(A.\overline{E}).(\overline{B}+\overline{C}.D)$
- $\mathbf{E.} \ \ (\mathbf{A} + \overline{\mathbf{E}}) + (\overline{\mathbf{B}}.(\overline{\mathbf{C}} + \mathbf{D}))$